
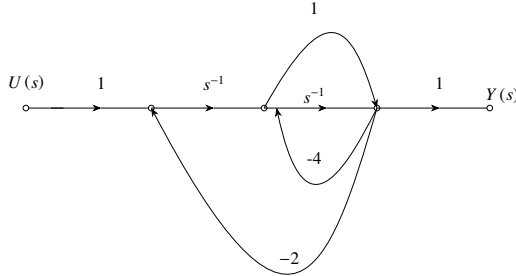


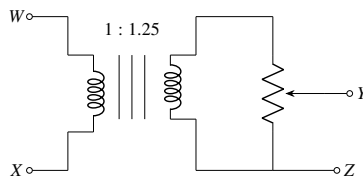- 1) The signal flow graph for a system is given below. The transfer function $\frac{Y(s)}{U(s)}$ for this system is.




- a) $\frac{s+1}{5s^2+6s+2}$ b) $\frac{s+1}{s^2+6s+2}$ c) $\frac{s+1}{s^2+4s+2}$ d) $\frac{1}{5s^2+6s+2}$
- 2) The impulse response of a continuous time system is given by $h(t) = \delta(t-1) + \delta(t-3)$. The value of the step response at $t = 2$ is.
- a) 0 b) 1 c) 2 d) 3
- 3) Two magnetically uncoupled inductive coils have Q factors q_1 and q_2 at the chosen operating frequency. Their respective resistances are R_1 and R_2 . When connected in series, their effective Q factor at the same operating frequency is.
- a) $q_1 R_1 + q_2 R_2$ b) $\frac{q_1}{R_2} + \frac{q_2}{R_2}$ c) $\frac{(q_1 R_1 + q_2 R_2)}{(R_1 + R_2)}$ d) $q_1 R_2 + q_2 R_1$
- 4) The following arrangement consists of an ideal transformer and an attenuator which attenuates by a factor of 0.8. An ac voltage $V_{WX1} = 100V$ is applied across WX to get an open circuit voltage V_{YZ1} across YZ . Next, an ac voltage $V_{YZ2} = 100V$ is applied across YZ to get an open circuit voltage V_{WX2} across WX . Then $\frac{V_{YZ1}}{V_{WX1}}, \frac{V_{WX2}}{V_{YZ2}}$




- a) $\frac{125}{100}$ and $\frac{80}{100}$ b) $\frac{100}{100}$ and $\frac{80}{100}$ c) $\frac{100}{100}$ and $\frac{100}{100}$ d) $\frac{80}{100}$ and $\frac{80}{100}$

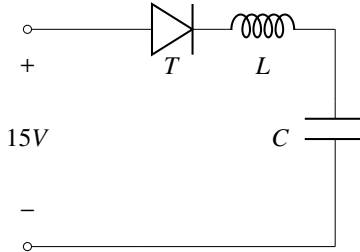- 5) Thyristor T in the figure below is initially off and is triggered with a single pulse of width $10\mu s$. It is given that $L = \left(\frac{100}{\pi}\right) \propto H$ and $C = \left(\frac{100}{\pi}\right) \propto F$. Assuming latching and holding currents of the thyristor are both zero and the initial charge on C is zero, T conducts for



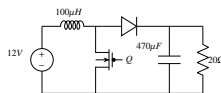- a) $10\mu s$ b) $50\mu s$ c) $100\mu s$ d) $200\mu s$
- 6) A 4-pole induction motor, supplied by a slightly unbalanced three-phase 50Hz source, is rotating at 1440rpm. The electrical frequency in Hz of the induced negative sequence current in the rotor is
- a) 100 b) 98 c) 52 d) 48
- 7) A function $y = 5x^2 + 10x$ is defined over an open interval $x = (1, 2)$. At least at one point in this interval, $\frac{dy}{dx}$ is exactly
- a) 20 b) 25 c) 30 d) 35
- 8) When the Newton-Raphson method is applied to solve the equation $f(x) = x^3 + 2x - 1 = 0$, the solution at the end of the first iteration with the initial guess value as $x_0 = 1.2$ is
- a) -0.82 b) 0.49 c) 0.705 d) 1.69
- 9) In the figure shown below, the chopper feeds a resistive load from a battery source. MOSFET Q is switched at 250kHz, with a duty ratio of 0.4. All elements of the circuit are assumed to be ideal.



The average source current in Amps in steady-state is


a) $\frac{3}{2}$

b) $\frac{5}{3}$

c) $\frac{5}{2}$

d) $\frac{15}{4}$

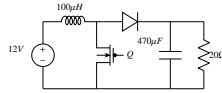- 10) In the figure shown below, the chopper feeds a resistive load from a battery source. MOSFET Q is switched at 250kHz, with a duty ratio of 0.4. All elements of the circuit are assumed to be ideal.



The Peak-to-Peak source current ripple in Amps is

a) 0.96

b) 0.144

c) 0.192

d) 0.288

- 11) The state variable formulation of a system is given as

$$\begin{pmatrix} \dot{x}_1 \\ \dot{x}_2 \end{pmatrix} = \begin{pmatrix} -2 & 0 \\ 0 & -1 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \end{pmatrix} + \begin{pmatrix} 1 \\ 1 \end{pmatrix} u, x_1(0) = 0, x_2(0) = 0 \text{ and } y = \begin{pmatrix} 1 & 0 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \end{pmatrix}$$

The system is

- a) controllable but not observable
- b) not controllable but observable
- c) both controllable and observable
- d) both not controllable and not observable

- 12) The state variable formulation of a system is given as

$$\begin{pmatrix} \dot{x}_1 \\ \dot{x}_2 \end{pmatrix} = \begin{pmatrix} -2 & 0 \\ 0 & -1 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \end{pmatrix} + \begin{pmatrix} 1 \\ 1 \end{pmatrix} u, x_1(0) = 0, x_2(0) = 0 \text{ and } y = \begin{pmatrix} 1 & 0 \end{pmatrix} \begin{pmatrix} x_1 \\ x_2 \end{pmatrix}$$

The response $y(t)$ to a unit step input is


a) $\frac{1}{2} - \frac{1}{2}e^{-2t}$

b) $1 - \frac{1}{2}e^{-2t} - \frac{1}{2}e^{-t}$

c) $e^{-2t} - e^{-t}$

d) $1 - e^{-t}$

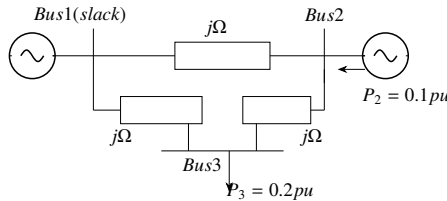- 13) In the following network, the voltage magnitudes at all buses are equal to $1p.u.$, the voltage phase angles are very small, and the line resistances are very negligible. All the line reactances are equal to $j\Omega$



a) $\theta_2 = -0.1, \theta_3 = -0.2$

c) $\theta_2 = 0.1, \theta_3 = 0.1$

b) $\theta_2 = 0, \theta_3 = -0.1$

d) $\theta_2 = 0.1, \theta_3 = 0.2$